

Either Dom doesn't play drums or Dom plays bass.

$$\sim p \vee q$$

Dom plays drums but not bass $p \wedge \sim q$

Dom doesn't play both drums and bass $\sim(p \wedge q)$


$$\sim p \vee \sim q$$

It is not the case that Dom plays drums but not bass.

$$\sim(p \wedge \sim q) \equiv \sim p \vee q$$

If Dom plays drums then he plays bass.




$$p \rightarrow q \equiv \sim p \vee q$$

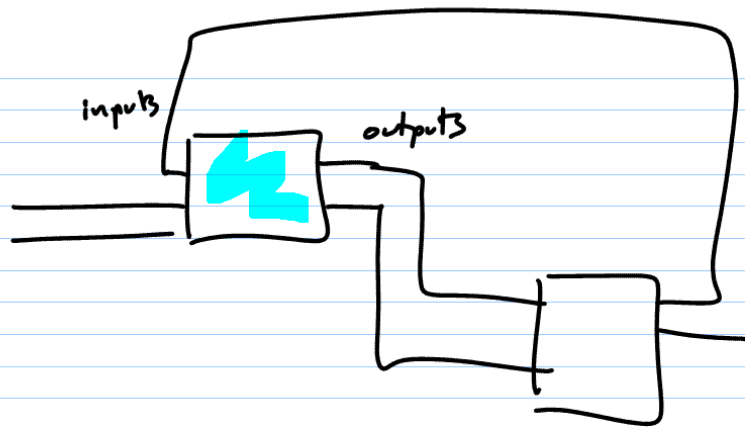

digital circuit: current on wire or not
(on / off)

black boxes: can describe behavior based
on what outputs are for
different inputs

basic logic boxes

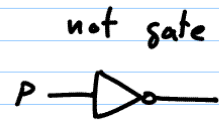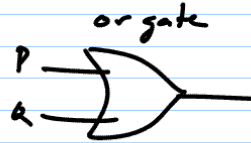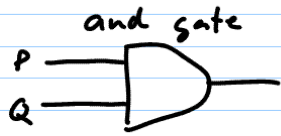

P	Q	output
1	1	1
1	0	0
0	1	0
0	0	0

P	Q	output
1	1	1
1	0	1
0	1	1
0	0	0


P	output
1	0
0	1

I/O tables



combinational circuit: can't combine inputs

can't connect output back to input

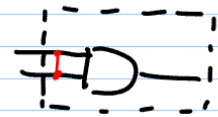
can have output of 1 gate as input of another



can split wires

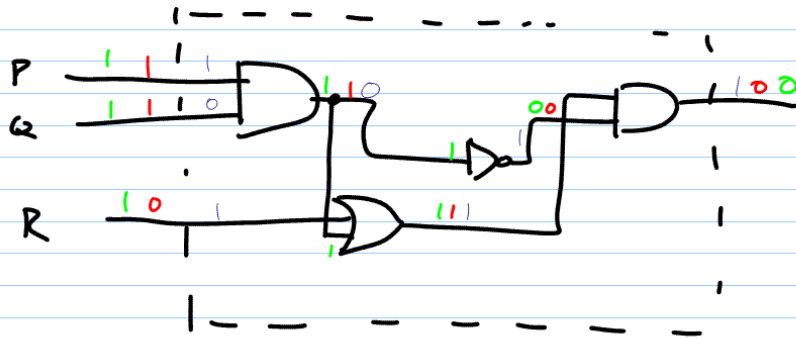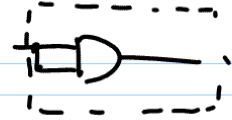


P	Q	R	output
1	1	0	0
1	0	0	0
0	0	0	0
0	0	1	0

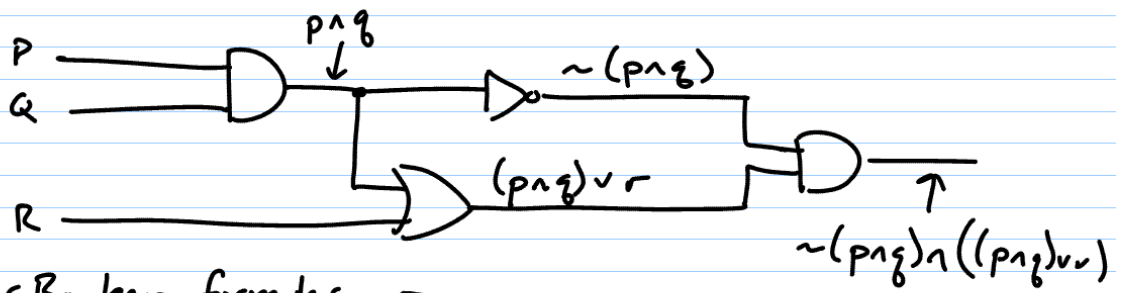

Boolean formulas
 ↓
 Combinational circuits
 ↓
 I/O table
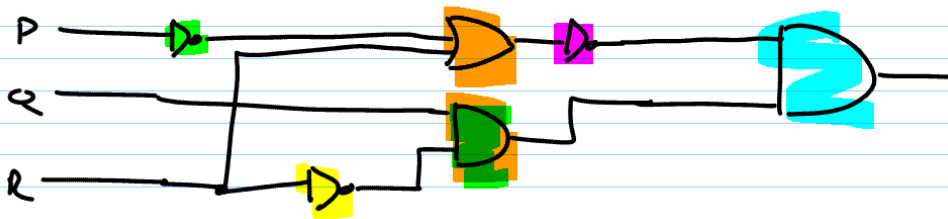
$$(\neg(\neg p \vee r)) \wedge (q \wedge \neg r)$$



I/O → circuit

1) pick rows where output on (1)

2) build recognizer for each row


↳ output is on for (recognizes)

exactly one combination of inputs

3) or outputs of recognizers together

3-input and

P	Q	R	output
1	1	1	0
1	0	1	0
1	0	0	1
0	1	0	1
0	0	1	0
0	0	0	0

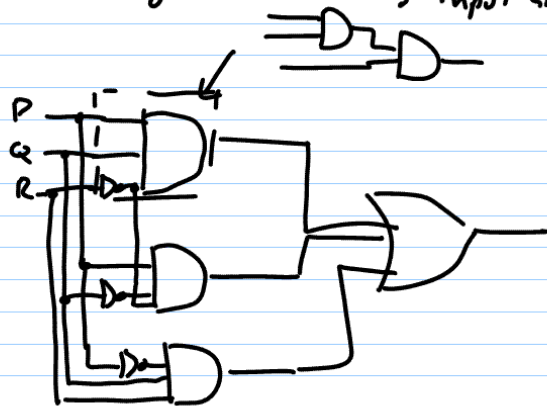

binary numbers allow integers to be encoded on wires

↳ use digits 0/1 in place value system

with place values = powers of 2

$$\begin{array}{r} \underline{3} \quad \underline{7} \quad \underline{1} \\ 100 \quad 10 \quad 1 \end{array} = 3 \cdot 100 + 7 \cdot 10 + 1 \cdot 1$$
$$= 3 \cdot 10^2 + 7 \cdot 10^1 + 1 \cdot 10^0$$

$$\begin{array}{r} \underline{1} \quad \underline{0} \quad \underline{1} \quad \underline{1} \quad \underline{0} \quad \underline{1} \quad \underline{0} \quad \underline{1} \\ 128 \quad 64 \quad 32 \quad 16 \quad 8 \quad 4 \quad 2 \quad 1 \end{array} = 1 \cdot 1 + 0 \cdot 2 + 1 \cdot 4 + 0 \cdot 8 + 1 \cdot 16 + 1 \cdot 32$$
$$+ 0 \cdot 64 + 1 \cdot 128$$
$$= 181$$



$$\begin{array}{r} 7 \\ + 364 \\ \hline 1 \end{array}$$

$7+4 = 11$

$$\begin{array}{r} 010011 \\ + 001001 \\ \hline 110110 \end{array}$$

101
39
220

$1+1 = 2 = 10_2$

P	Q	carry	sum
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	0

I/O table for half-adder